

# **Wave Shaping Circuits**

## **Sawtooth Generator**

**AET 11**

**Courtesy of the United States Air Force**


## **3c. Identify Sawtooth Generator Operating Principles**

# SAWTOOTH

- PURPOSE – To produce a sawtooth waveform. One input cycle will produce one output cycle.
- Also known as sweep, time/base, time/division, seconds/division, or ramp generator.
- This circuit is considered a relaxation oscillator.

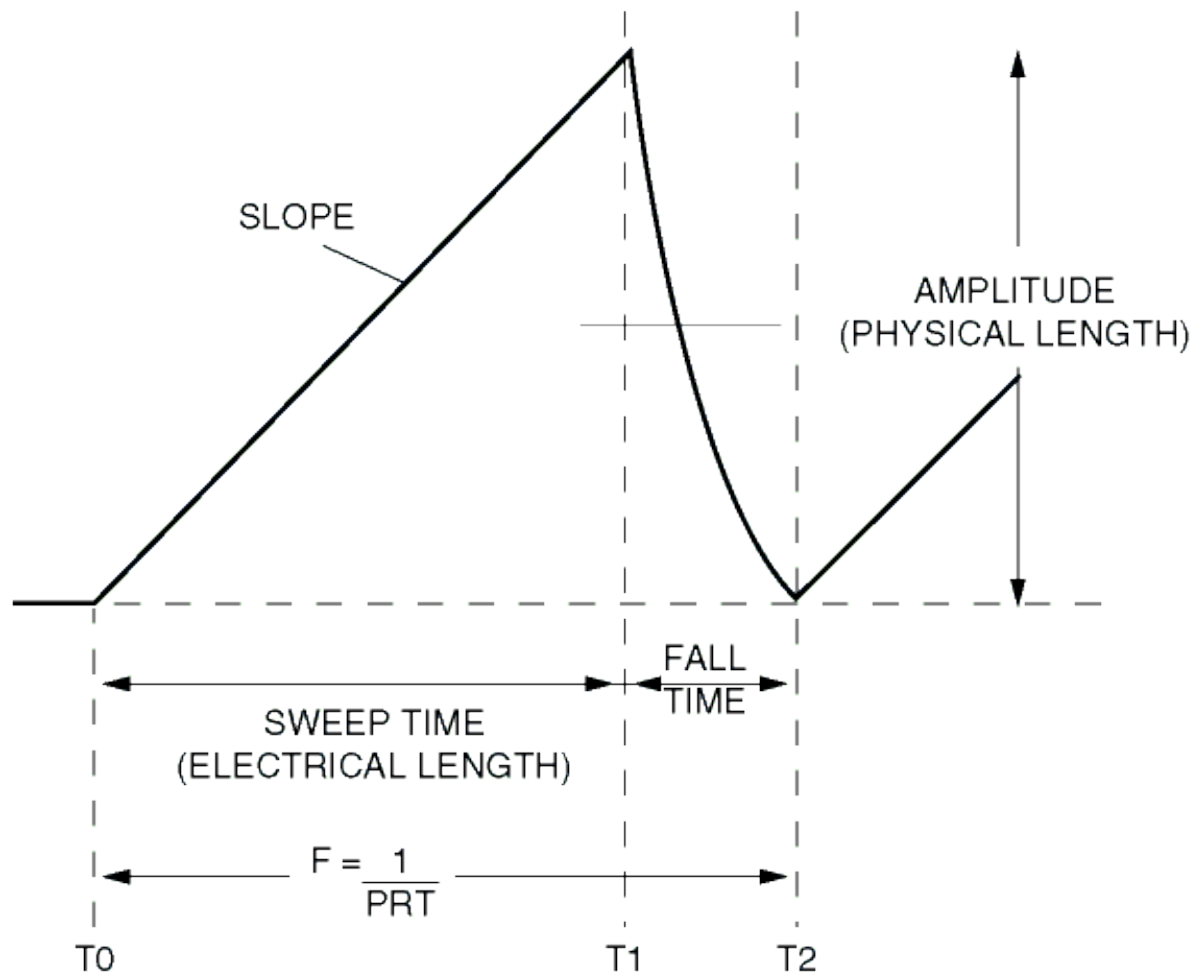
# Parts of sawtooth waveform

- Sweep time/electrical length  
(Time allowed to charge)
- Rest or flyback time (Discharge Time)
- Physical length (Amplitude)
- Slope (Rate of rise/percent of curve)
- PRT
- PRF




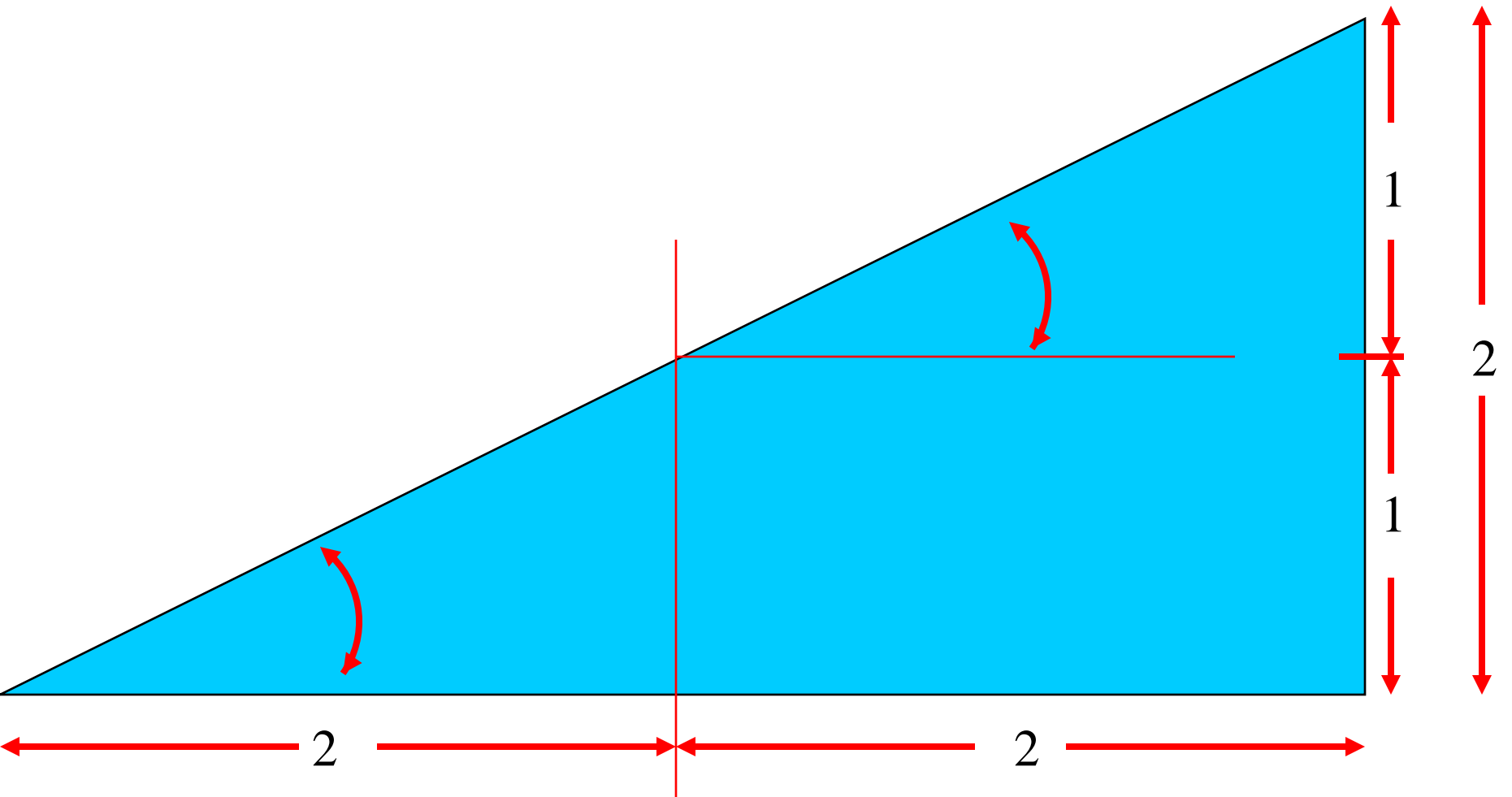**Sawtooth Waveform**


The Sawtooth Generator, produces a waveform that will have a linear rise characteristic. RISE over RUN  
**SLOPE**



# Simple Sawtooth Circuit


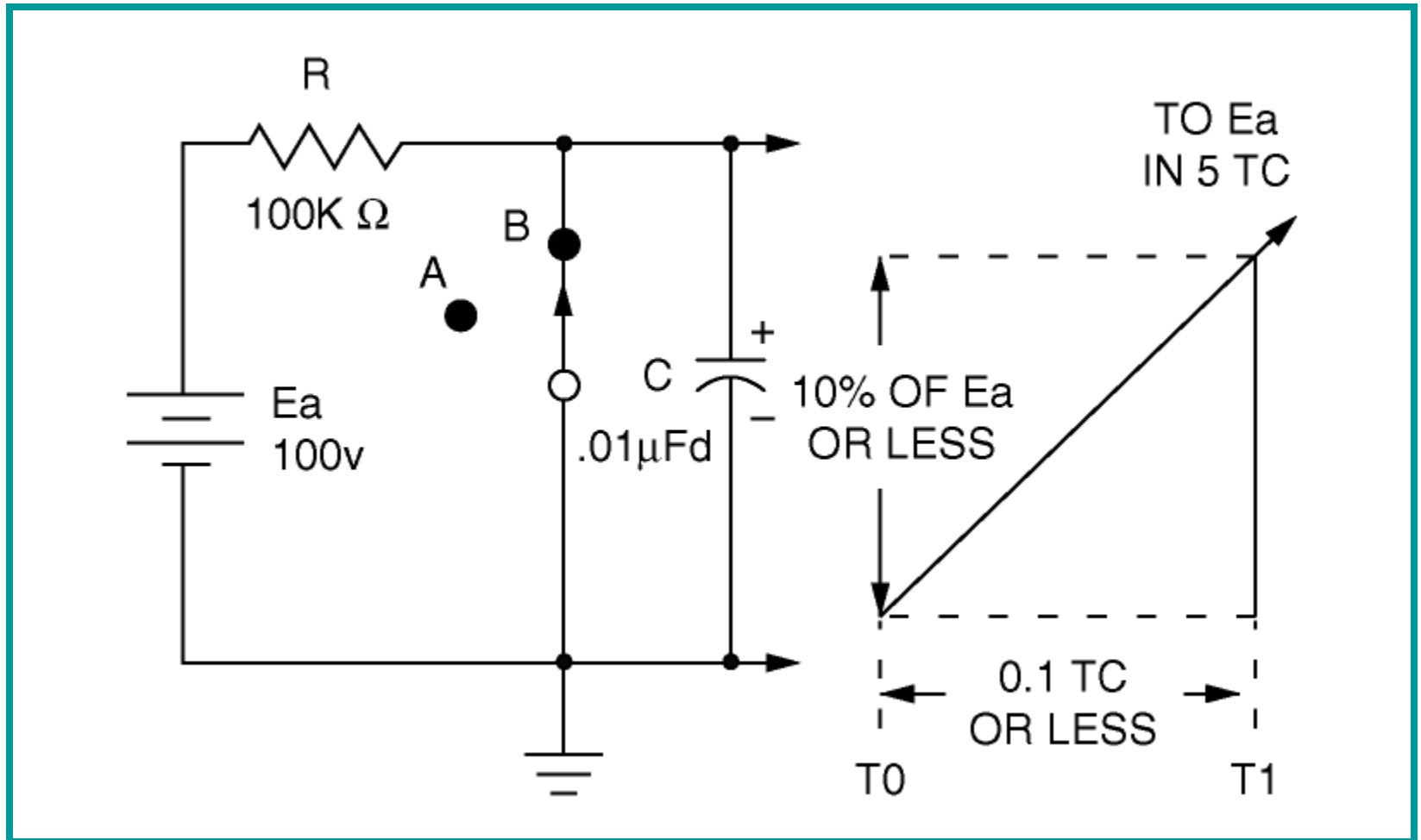


# Universal Time Constant Chart

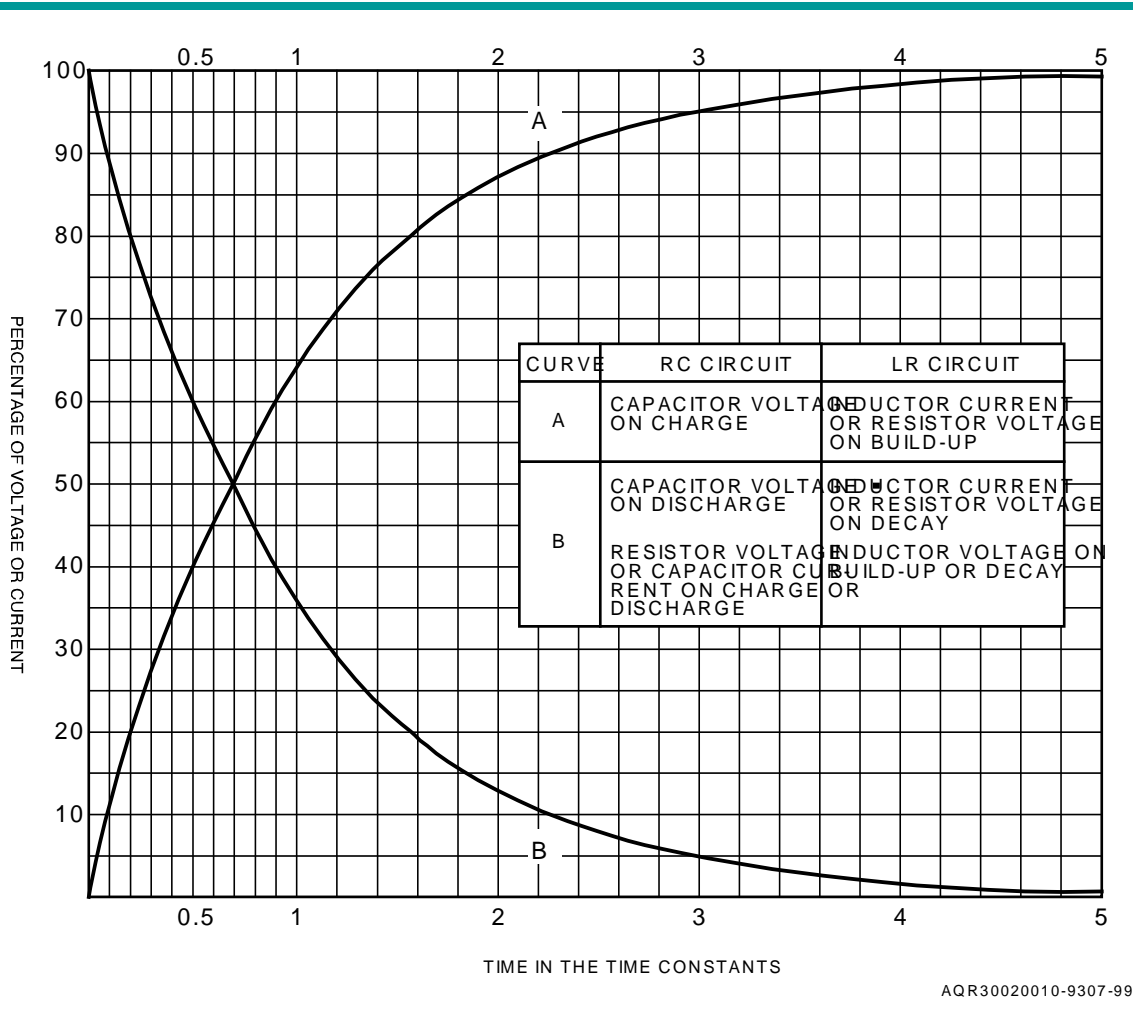

Referring to the Universal Time Constant Chart, you will find that the most linear part of the curve is the first 10% of the first time constant.

# Sawtooth Generator

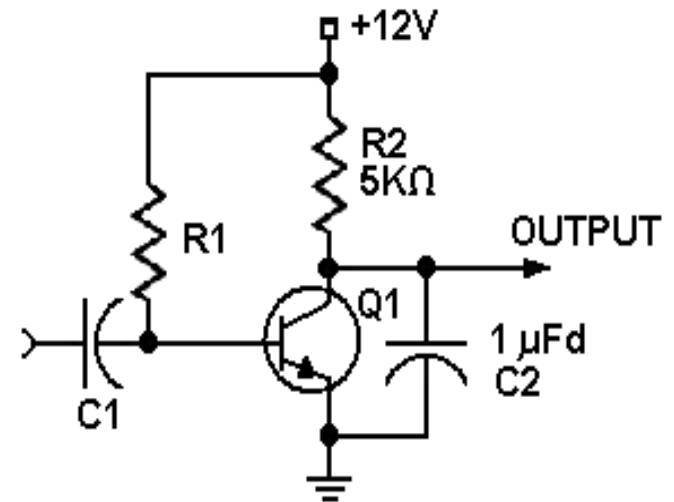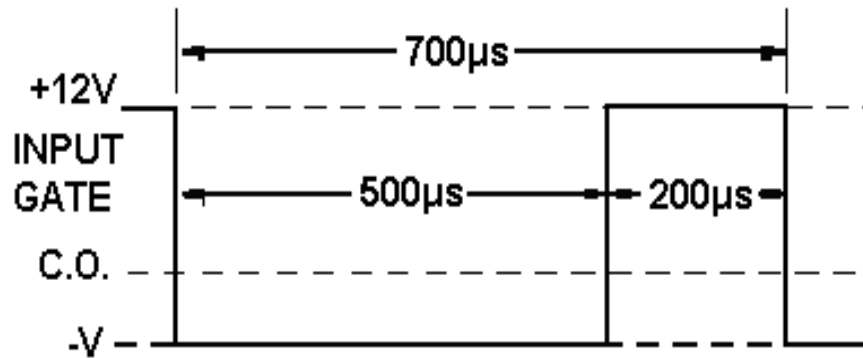


# Purpose of Components

- ☛ R1 – Provides forward bias for Q1.
- ☛ C1 – Input signal coupling capacitor
- ☛ Q1 – Serves as charge and discharge switch for the RC network consisting of R2 and C2.
- ☛ R2/C2 – RC network that produces the slope/ramp portion of the output wave.


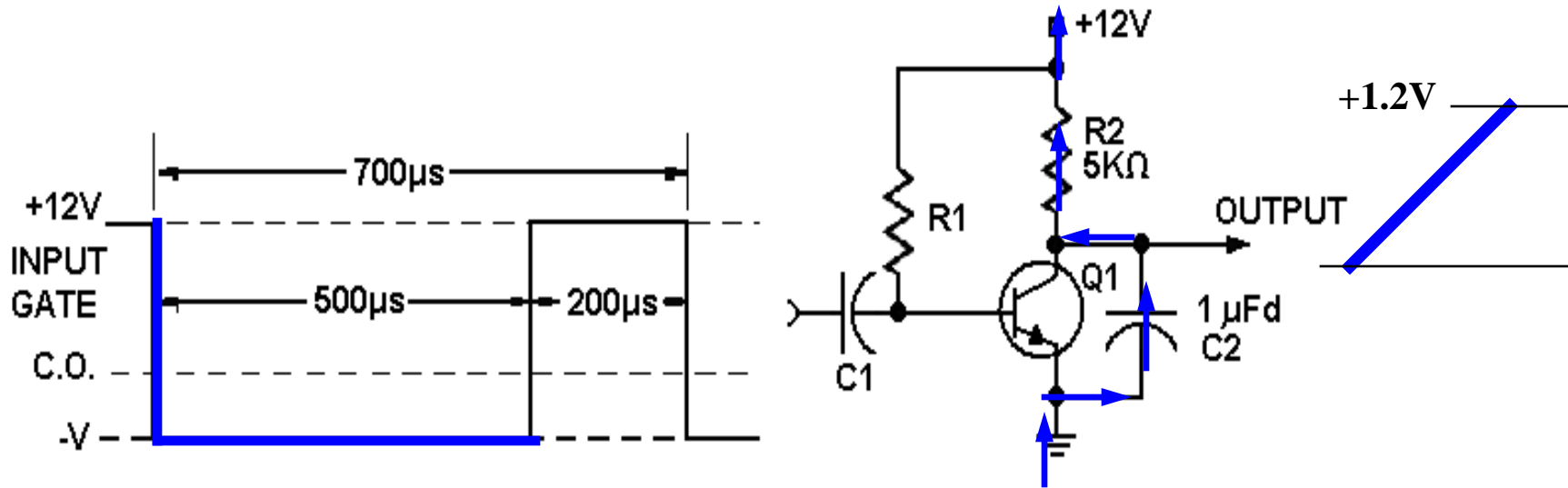
# Sawtooth Generator Operation

C2 charges through R2 developing the output slope when Q1 is cutoff by the negative gate.


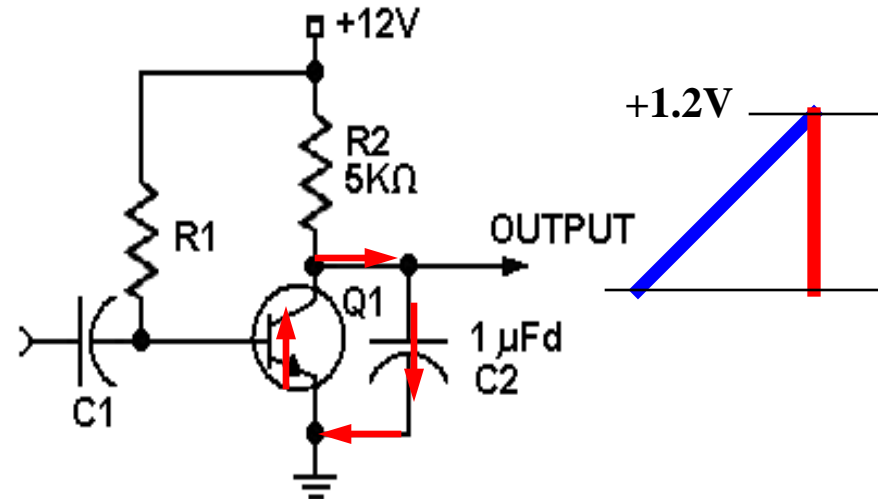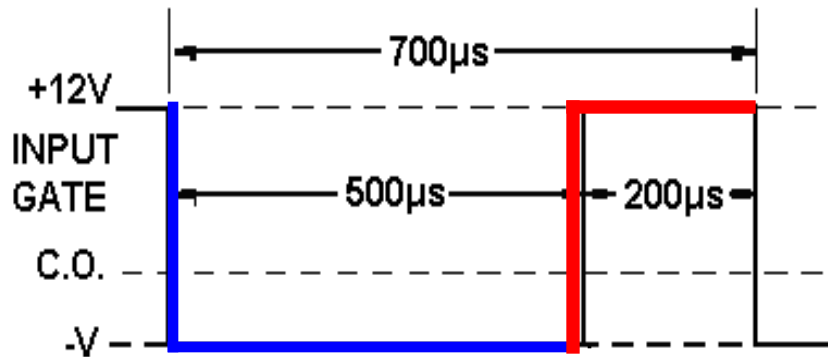
# Sawtooth Generator Operation

**C2 discharges** through **Q1** when **Q1** is **saturated** (conducting) by the positive gate and this is the flyback time.




# Relationships


$$\textit{Amplitude} = \frac{\textit{NegativeGateLength}}{\textit{RC}}$$

$$\textit{Linearity} = \frac{\textit{RC}}{\textit{NegativeGateLength}}$$

# Gate Length – Linearity Relationship

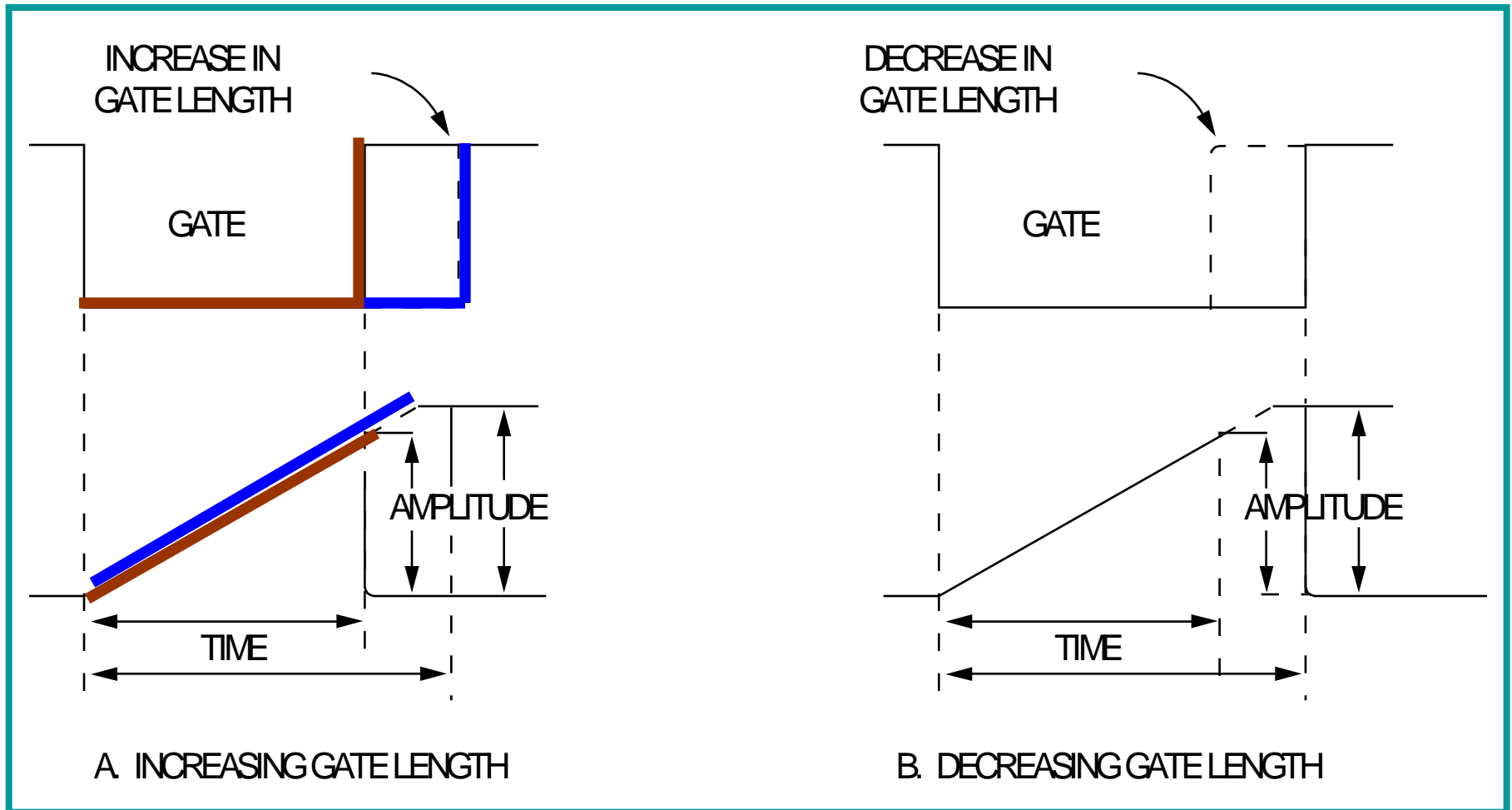


# RC – Linearity Relationship

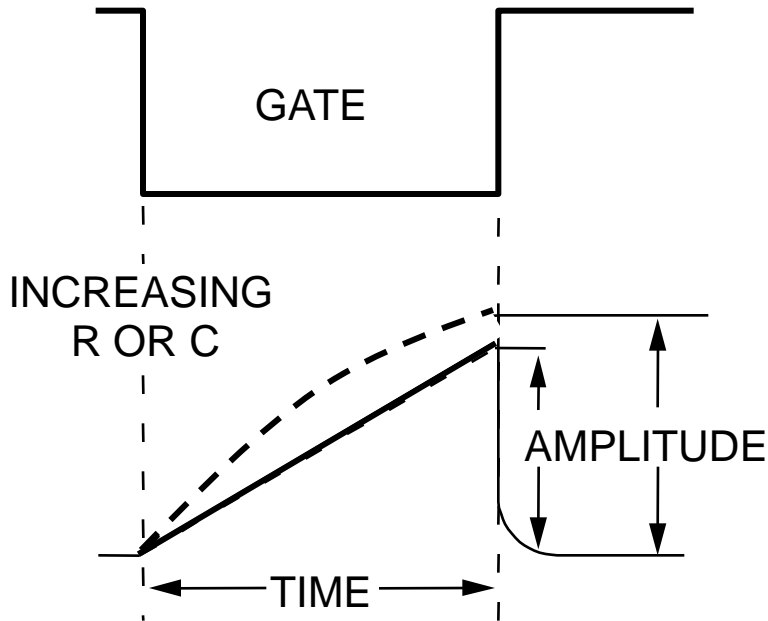

A. INCREASING R or C

Increases Linearity

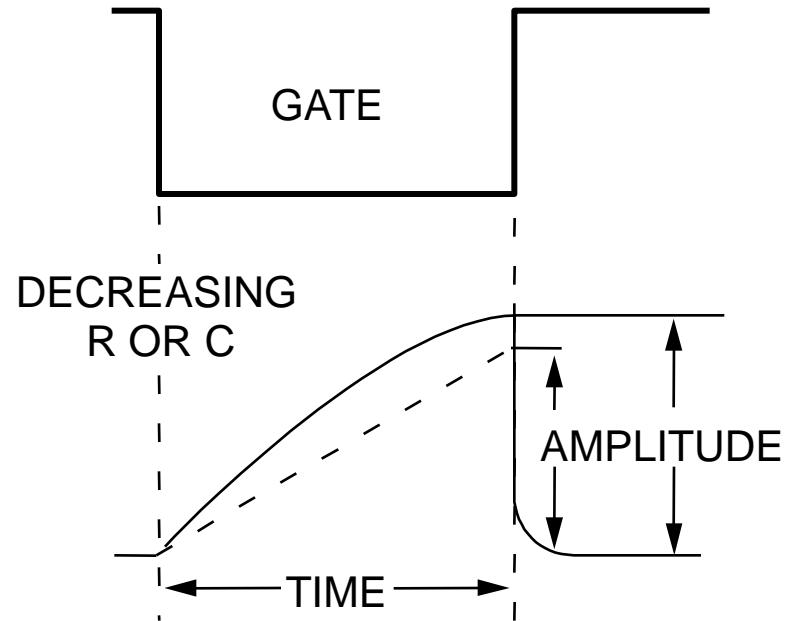

B. DECREASING R or C

Decreases Linearity

..... Before

———— After



# Block 5

## **Summary 3c**

- Parts of the Waveform
- Sawtooth Generator components
- Circuit operation
- Parameter Changes



# **Sawtooth Generator Appraisal**

# Sawtooth Generator

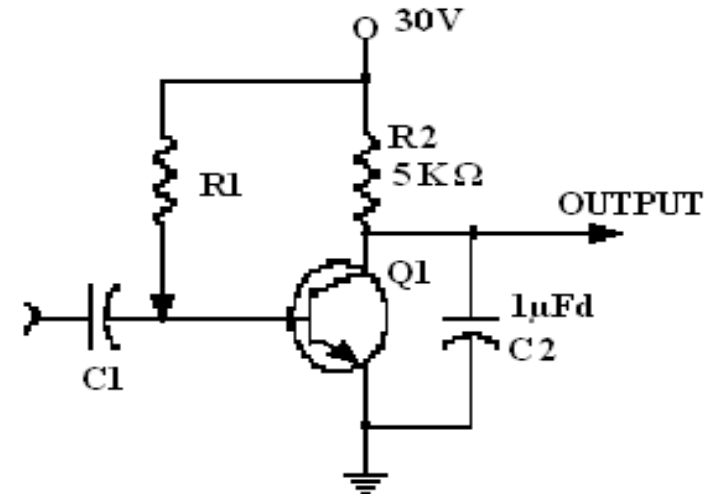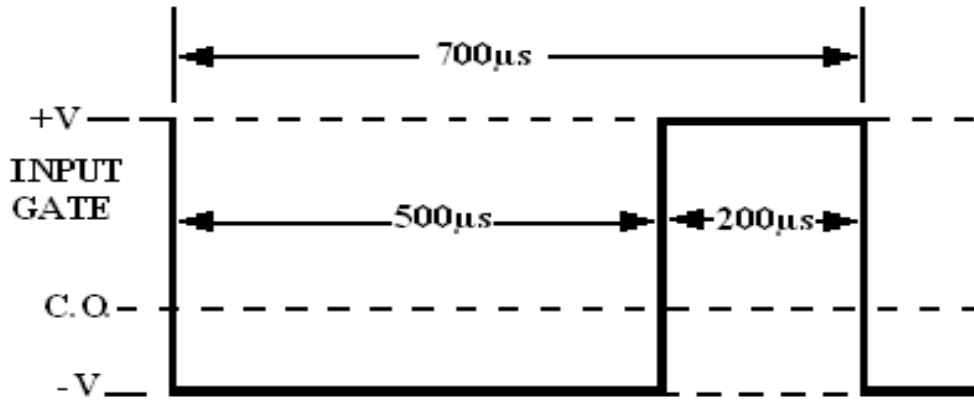

1. In the sawtooth generator circuit, a positive gate applied to the base of Q1 will \_\_\_\_\_ C2.
  - a. charge
  - b. discharge



# Sawtooth Generator

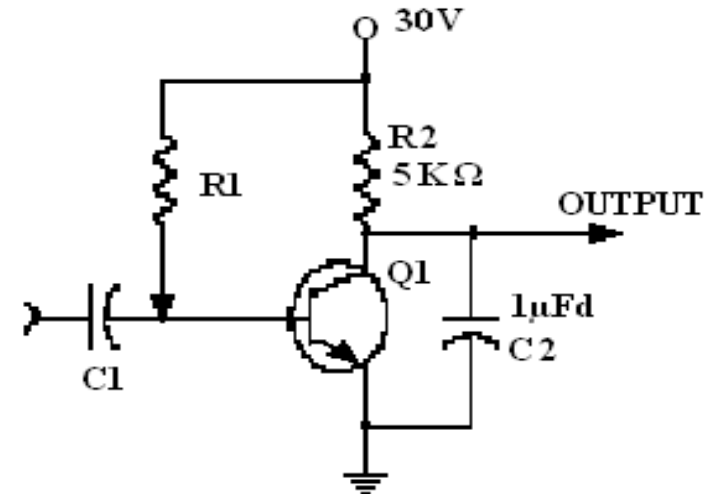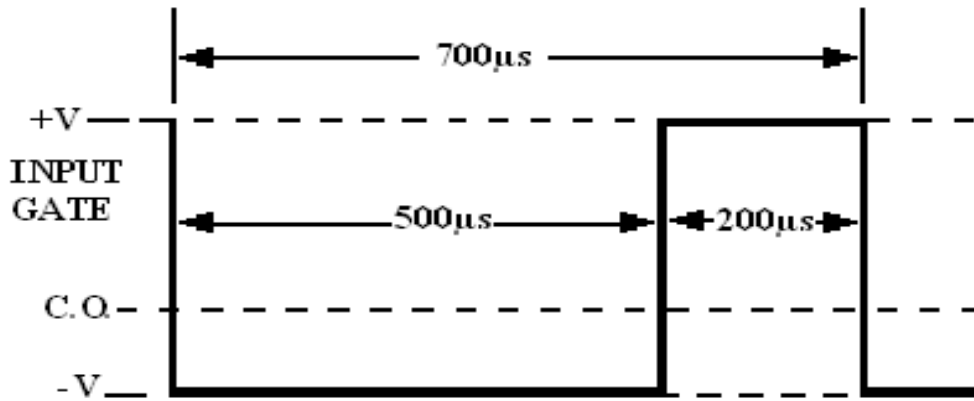

2. In the sawtooth generator circuit, the rate of voltage change across capacitor  $C2$  is almost linear during the first \_\_\_\_\_ of the capacitor charge time.



- a. 1%
- b. 5%
- c. 10%
- d. 20%

# Sawtooth Generator

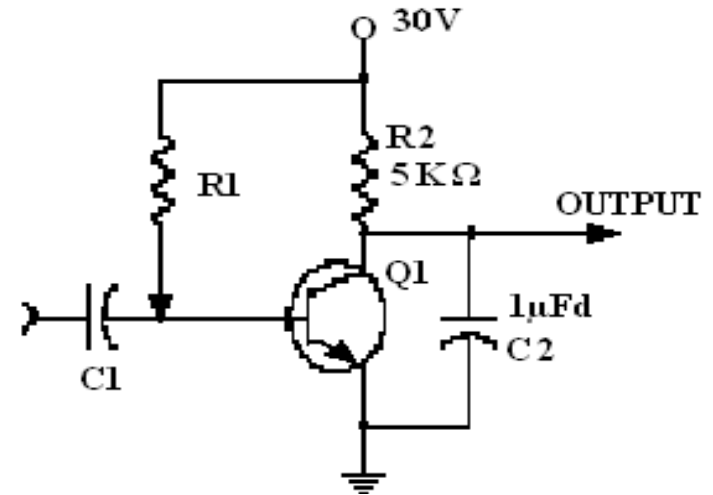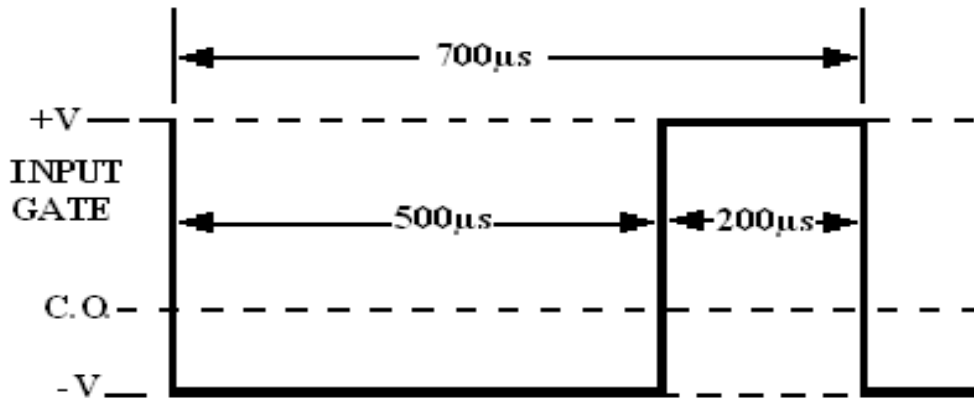

3. The linearity of the sawtooth waveform is controlled by
- $R2$
  - $C2$
  - negative input gate duration
  - all of the above

# Sawtooth Generator

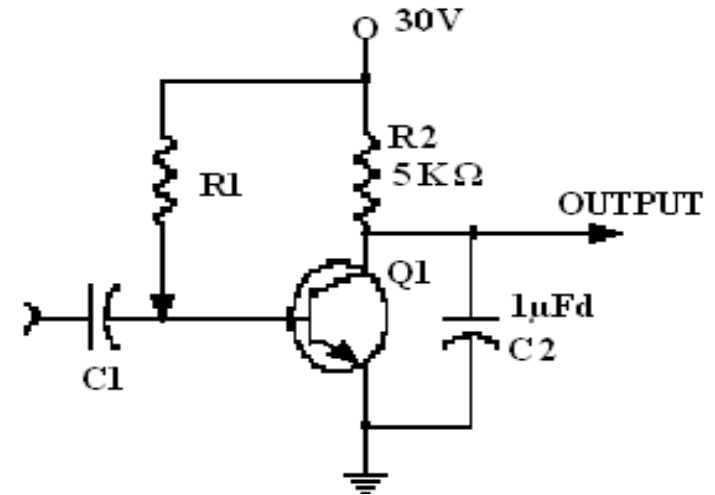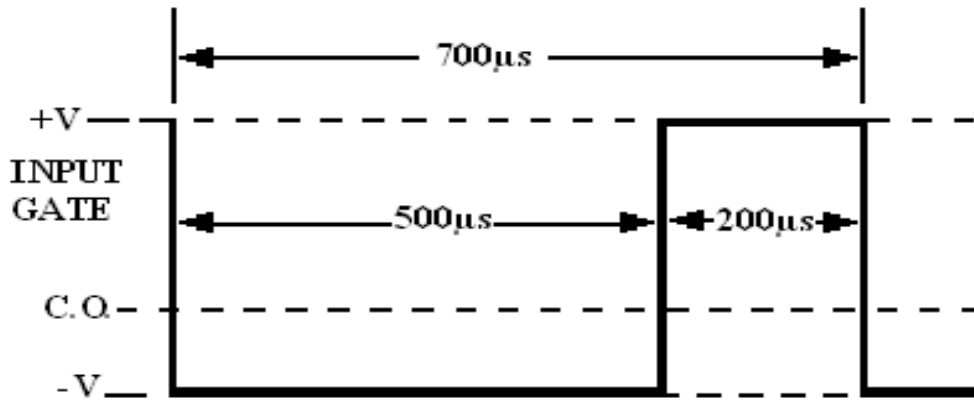

4. A negative gate applied to the base of Q1 will \_\_\_\_\_ Q1 and allow C2 to \_\_\_\_\_ through R2.
- cutoff; charge
  - cutoff; discharge
  - saturate; charge
  - saturate; discharge

# Appraisal Answers

**1. B**

**2. C**

**3. D**

**4. A**